

# 272-Q21

## BCTHS MECHATRONICS TECHNOLOGY

NAME: \_\_\_\_\_

START DATE: \_\_\_\_/\_\_\_\_/\_\_\_\_

COMPLETION DATE: \_\_\_\_/\_\_\_\_/\_\_\_\_

**TASK:** *Switched mode power supply theory*

**PERFORMANCE OBJECTIVE:** *Given a written test, the student will identify the areas and components of a switched mode power supply with at least 75% accuracy.*

**ENABLING OBJECTIVE:** *Complete Q01 – Q20*

**TOOLS REQUIRED:** *SMPS and Power supply theory video and instructor lecture*

**SAFETY FACTORS:** *Complete Q01-Q02 and observe all school/classroom safety rules at all times*

### **ACADEMIC ANCHORS:**

*M11.A.1.1.2 Express numbers using scientific notation*

*M11.A.2.1.1 Solve problems operations with rational numbers using rates and percentages*

*M11.A.2.1.2 Solve problems using direct and inverse proportions*

*R11.A.1.3.5 Demonstrate after reading understanding of non-fiction text*

*R11.A.2.1.2 Identify meaning of content specific words used in text*

### **CAREER & WORK ANCHORS:**

*13.2.11.E Demonstrate essential workplace skills.*

### **PERFORMANCE CHECKLIST:**

<b>STUDENT CHECK</b>	<b>TASK TO BE COMPLETED</b>	<b>TEACHER SIGN OFF</b>
	1. Identify academic anchors and complete learning guide AA01	_____
	2. Read info and Safety sheets	_____
	3. Complete Performance Sheets	_____
	4. Take written exam	_____

### **PERFORMANCE LEVEL:**

**MASTERY      SATISFACTORY      FAMILIARIZATION      INSTRUCTED/CANNOT PERFORM**

BUCKS COUNTY TECHNICAL SCHOOL – June 17, 2021

\_\_\_\_\_  
**INSTRUCTOR'S SIGNATURE**

## **272-Q21**

### **Safety and information sheet**

Follow all electrical safety rules when building, servicing, or making measurements in any power supply. Power supplies contain lethal voltages. Always work with someone near by. Always make sure capacitors are discharged when the unit is unplugged as it may still have lethal voltage.

Power supplies are used in almost every electronic device that is not battery powered. Their purpose is to take standard line voltage (120 V.A.C.) and convert it to the needed voltage for a device. They may also convert the voltage to D.C. and provide regulation.

**272-Q20**

## **PERFORMANCE SHEET**

1. Why are Switched Mode Power Supplies (SMPS) sometimes called DC to DC converters?
2. How does a SMPS regulate voltage?
3. What is an OPTO coupler, OPTO Isolator, or photo coupler?
4. Why must a SMPS have a line choke?
5. What kind of protective devices does a SMPS utilize and why?
6. What circuit or components start the switch mode cycle?

7. Why does the switching cycle vary frequency and duty cycle?

8. Why do most SMPS's use half wave rectifiers on the secondary?

List 2 advantages and disadvantages of the SMPS over the standard transformer rectifier power supply.

9.

10.

11.

12.

13. How does troubleshooting the SMPS differ from troubleshooting the standard power supply?

## GRADING RUBRIC

	Instructed/Cannot 0 points	Familiarization 1 point	Satisfactory 2 points	Mastery 3 points
Safety	Student rarely follows industry standard safety rules	Student needs to be frequently reminded to follow industry standard safety rules	Follows all industry standard safety rules, but required one reminder.	Student always follows all industry standard safety rules
Task	Student is unable to complete task	Student requires frequent assistance to complete task, and/or is familiar with some parts of the task	Student requires very little assistance to complete task, or has only completed task once or twice, but completed it satisfactorily with little to no assistance	Student can perform task with no assistance and has completed the task many times with no errors.

Mastery = 6 points

Satisfactory = 4-5 points

Familiarization = 2-3 points

Instructed cannot perform = <2 points